

Experiment 10: Tone Generator

Annirudh K P

210070009

October 22, 2022

1 Overview of the experiment

In this experiment, we worked on some sequential circuit designs using behavioural modelling on VHDL. The problem statement of this experiment is to design a Tone Generator using the already acquired knowledge of Clock Divider from the previous lab. The objective of this experiment is to understand the Quartus Design Flow, work with the Xen10 Board, use Pin Planning, and give us hands on experience over different technical glitches/problems we may face in this piece of software which has been made unwantedly hard.

2 Experimental Set-up

2.1 Design Schematics

The idea behind the design of Clock divider, which is to be used for the tone generator is as shown:

Method to generate any arbitrary frequency from 50 MHz clock

Suppose you want to generate the frequency of $f = 10$ Hz.

$$count = 50MHz / (2 * f)$$

Further the set of frequencies and counts used for the tone generator are as follows:

Table 1: Frequency Table

Note	Frequency(Hz)	Count Value
Sa	240	104168
Re	270	92584
Ga	300	83333
Ma	320	78125
Pa	360	69444
Dha	400	62500
Ni	450	55554
Sa (upper octave)	480	52084

2.2 Description of Components

2.2.1 Clock Divider

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity tone_generator is
port (clk_50 : in std_logic;
switch : in std_logic_vector(7 downto 0);
LED_out : out std_logic_vector(7 downto 0);
final_out : out std_logic);
end entity tone_generator;

architecture bhv of tone_generator is
signal count0, count1, count2, count3, count4, count5,
count6, count7 : integer := 1;
signal clk_out_temp : std_logic_vector(7 downto 0) := "00000000";

begin

```

```

clock_proc:process(clk_50)
begin
if(clk_50='1' and clk_50' event) then
count0 <= count0 + 1;
count1 <= count1 + 1;
count2 <= count2 + 1;
count3 <= count3 + 1;
count4 <= count4 + 1;
count5 <= count5 + 1;
count6 <= count6 + 1;
count7 <= count7 + 1;

if (count0 = 104168) then
count0 <= 1;
clk_out_temp(0) <= not clk_out_temp(0);
end if;
if (count1 = 92584) then
count1 <= 1;
clk_out_temp(1) <= not clk_out_temp(1);
end if;
if (count2 = 83333) then
count2 <= 1;
clk_out_temp(2) <= not clk_out_temp(2);
end if;
if (count3 = 78125) then
count3 <= 1;
clk_out_temp(3) <= not clk_out_temp(3);
end if;
if (count4 = 69444) then
count4 <= 1;
clk_out_temp(4) <= not clk_out_temp(4);
end if;
if (count5 = 62500) then
count5 <= 1;
clk_out_temp(5) <= not clk_out_temp(5);
end if;
if (count6 = 55554) then
count6 <= 1;

```

```

clk_out_temp(6) <= not clk_out_temp(6);
end if;
if (count7 = 52084) then
count7 <= 1;
clk_out_temp(7) <= not clk_out_temp(7);
end if;
end if;

LED_out <= "00000000";
if ((switch(0) and (not switch(1)) and (not switch(2)) and (not switch(3)) and
(not switch(4)) and (not switch(5)) and (not switch(6)) and (not switch(7))) = '1')
LED_out <= "00000000";
LED_out(0) <= '1';
final_out <= clk_out_temp(0);
elsif ((switch(0) and (switch(1)) and (not switch(2)) and (not switch(3)) and
(not switch(4)) and (not switch(5)) and (not switch(6)) and (not switch(7))) = '1')
final_out <= clk_out_temp(1);
LED_out <= "00000000";
LED_out(1) <= '1';
elsif ((switch(0) and (switch(1)) and (switch(2)) and (not switch(3)) and (not swi
and (not switch(5)) and (not switch(6)) and (not switch(7))) = '1') then
final_out <= clk_out_temp(2);
LED_out <= "00000000";
LED_out(2) <= '1';
elsif ((switch(0) and (switch(1)) and (switch(2)) and (switch(3)) and (not switch
and (not switch(5)) and (not switch(6)) and (not switch(7))) = '1') then
final_out <= clk_out_temp(3);
LED_out <= "00000000";
LED_out(3) <= '1';
elsif ((switch(0) and (switch(1)) and (switch(2)) and (switch(3)) and (switch(4))
and (not switch(5)) and (not switch(6)) and (not switch(7))) = '1') then
final_out <= clk_out_temp(4);
LED_out <= "00000000";
LED_out(4) <= '1';
elsif ((switch(0) and (switch(1)) and (switch(2)) and (switch(3)) and (switch(4))
and (switch(5)) and (not switch(6)) and (not switch(7))) = '1') then
final_out <= clk_out_temp(5);
LED_out <= "00000000";

```

```

LED_out(5) <= '1';
elsif ((switch(0) and (switch(1)) and (switch(2)) and (switch(3)) and (switch(4))
and (switch(5)) and (switch(6)) and (not switch(7))) = '1') then
final_out <= clk_out_temp(6);
LED_out <= "00000000";
LED_out(6) <= '1';
elsif ((switch(0) and (switch(1)) and (switch(2)) and (switch(3)) and (switch(4))
and (switch(5)) and (switch(6)) and (switch(7))) = '1') then
final_out <= clk_out_temp(7);
LED_out <= "00000000";
LED_out(7) <= '1';
else
final_out <= '0';
LED_out <= "00000000";
end if;

end process;
end bhv;

```

3 Observations

The code after appropriate pin planning, (in form of .svf file) was flashed onto the Xen10 board. Then like a keyboard, the LEDs are planned to blink when the respective key is played. The Header 1 Pin 1 is planned to give the output frequency according to the switch configuration. Using transistor, breadboard and a speaker, the circuit was set up. The output was verified, which also verified the working of the logic for the Tone Generator.

 


Figure 1: Tone Generator Circuit 1

 


Figure 3: Tone Generator Circuit 3